

第十五讲

第六部分 MIPS处理器设计

- 一. 处理器设计概述
- 二. MIPS模型机
- 三. MIPS单周期处理器设计
- 四. MIPS流水线处理器设计


洗衣房：生活中的流水线

- 处理器：洗衣房
- 4条指令：张、李、王、周
 - 指令：洗衣服
 - 指令过程：洗涤→烘干→熨整
- 指令各阶段延迟
 - 洗衣：30分钟
 - 烘干：40分钟
 - 熨整：20分钟




3

串行洗衣房

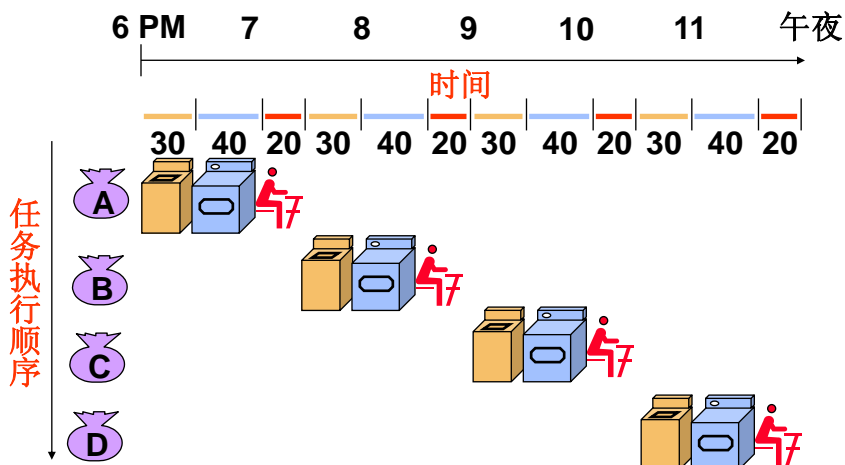

- 串行洗衣房：6个小时完成4个任务
- 如果采用流水线技术，那么。。。


流水化洗衣房：尽可能早地开始工作

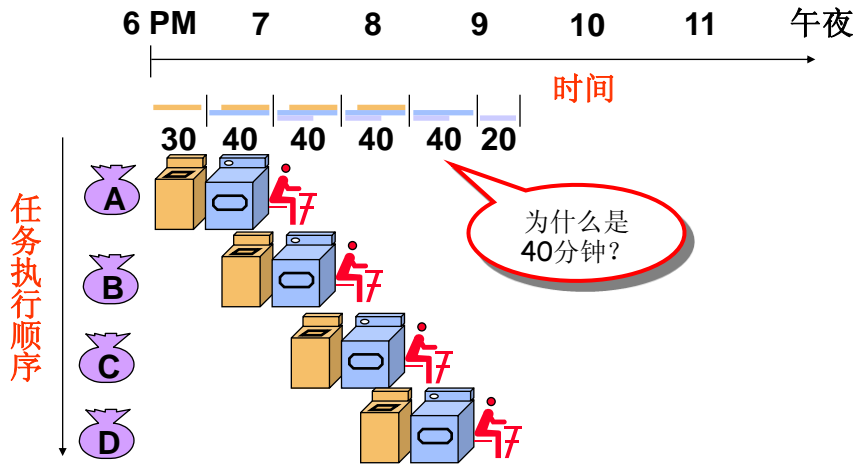

- 流水化洗衣房：3.5小时完成4个任务

5

流水线性质

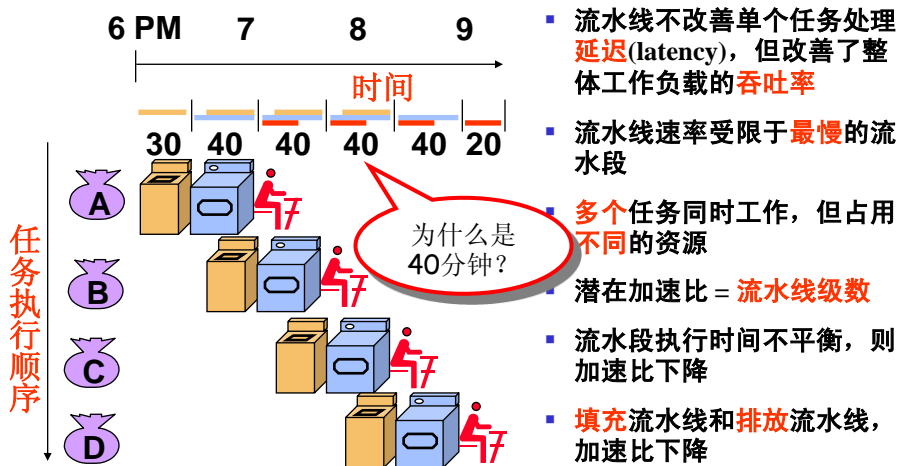

- 流水线不改善单个任务处理延迟(latency)，但改善了整体工作负载的吞吐率
- 流水线速率受限于最慢的流水段
- 多个任务同时工作，但占用不同的资源
- 潜在加速比 = 流水线级数
- 流水段执行时间不平衡，则加速比下降
- 填充流水线和排放流水线，加速比下降

6

Recall: 5 Stages of MIPS Datapath


- 1) **IF**: Instruction Fetch, Increment PC
- 2) **ID**: Instruction Decode, Read Registers
- 3) **EX**: Execution (ALU)
Load/Store: Calculate Address
Others: Perform Operation
- 4) **MEM**:
Load: Read Data from Memory
Store: Write Data to Memory
- 5) **WB**: Write Data Back to Register

7/24/2012

Summer 2012 -- Lecture #21

7

Pipelined Datapath

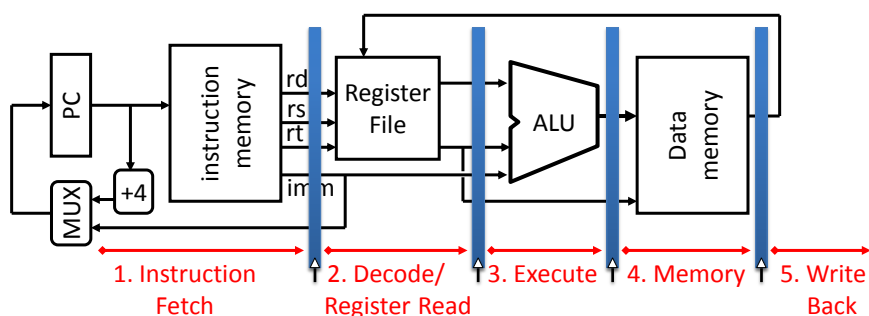

- Add registers between stages
 - Hold information produced in previous cycle
- 5 stage pipeline
 - Clock rate *potentially* 5x faster


7/24/2012

Summer 2012 -- Lecture #21

8


流水的控制信号

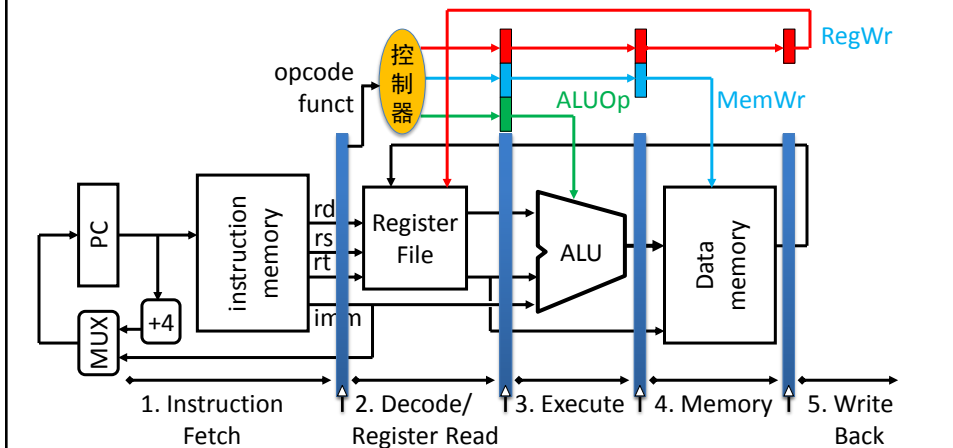- 控制器：译码产生控制信号，与单周期完全相同
- 控制信号流水寄存器：控制信号在寄存器中传递，直至不再需要




正确认识流水线—流水线寄存器

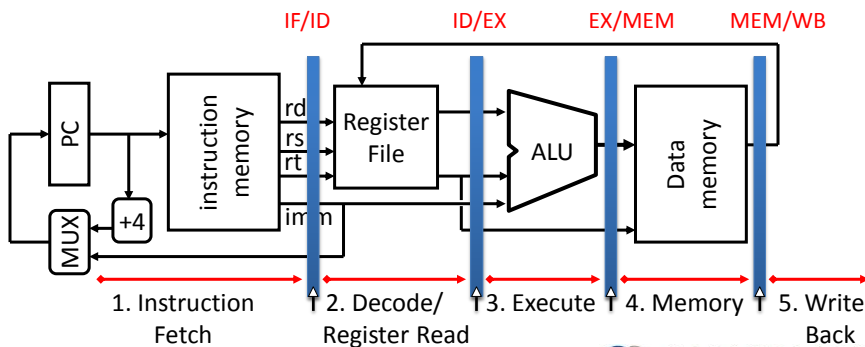- 命名法则：前级/后级
 - ◆ 示例：IF/ID，前级为读取指令，后级为指令译码(及读操作数)
- 功能：时钟上升沿到来时，保存前级结果；之后输出至下级组合逻辑
 - ◆ 也可能直接连接到下级流水线寄存器
 - 例如ID/EX保存的从RF读出的第2个寄存器值，就直接传递到EX/MEM



正确认识流水线—流水线级数与RF

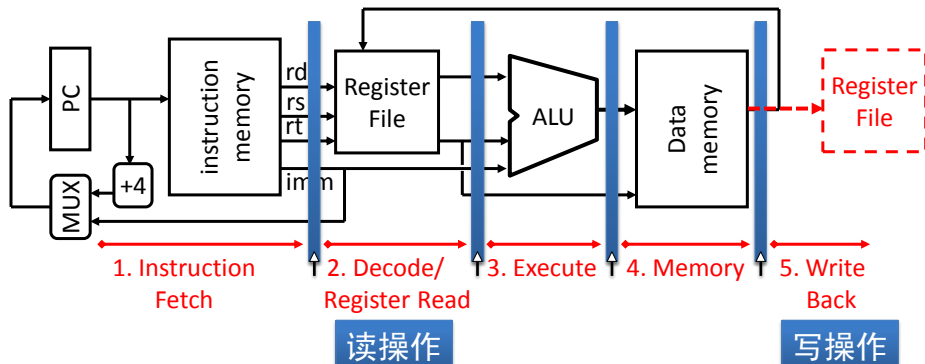
- N级流水线：必须有N级流水线寄存器
 - ◆ 插入N-1级流水线寄存器，最后一级为Register File
- RF：这是一个特殊部件，有2次使用
 - ◆ 读：第2级；写：第5级




11

北京航空航天大学计算机学院
School of Computer Science and Engineering, Beihang University

正确认识流水线：流水线级数与RF

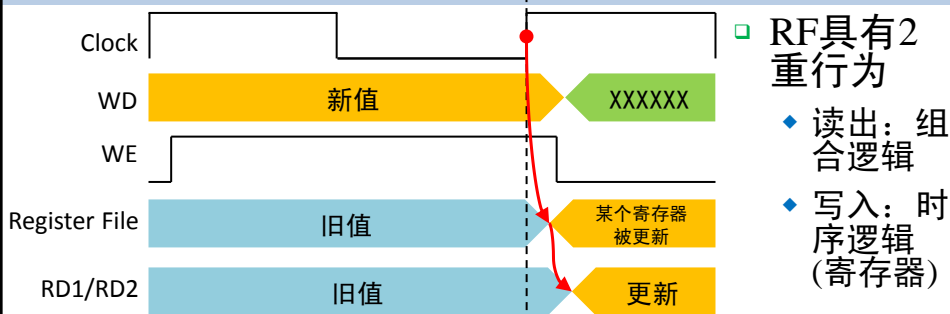

 - 写入：RF上升沿被更新
 - ◆ WE有效，上升沿时，WD被写入A3地址对应的Register
- 输出：与时钟无关，仅与RF内容及A1/A2相关




12

写入

读出

正确认识流水线：流水阶段与流水线寄存器

 
- 流水阶段：组合逻辑+寄存器
 - ◆ 起始：前级流水线寄存器的输出
 - ◆ 中间：组合逻辑（如ALU）
 - ◆ 结束：写入后级流水线寄存器
 - ◆ 当时钟上升沿到来时，组合逻辑计算结果存入后级寄存器
- 示例：EX阶段
 - ◆ 起始：ID/EX流水线寄存器中的RF寄存器/扩展单元的输出
 - ◆ 中间(组合逻辑)：ALU完成计算
 - ◆ 结束(寄存器)：在clock上升沿到来时，结果写入EX/MEM中相应寄存器



13

正确认识流水线：DM

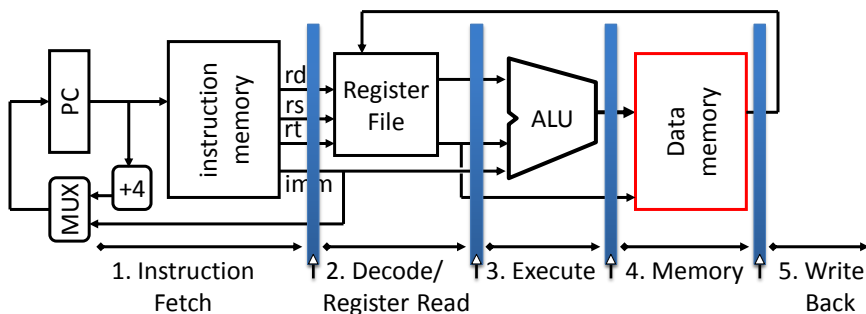- 写入时：表现为寄存器
 - ◆ 属于MEM/WB寄存器范畴
- 读出时：可等价为组合逻辑
 - ◆ 与RF的读出是类似的



14

Pipelining Changes

- Registers affect flow of information
 - Name registers for adjacent stages (e.g. IF/ID)
 - Registers *separate* the information between stages
 - At any instance of time, each stage working on a *different* instruction!
- Will need to re-examine placement of wires and hardware in datapath


7/24/2012

Summer 2012 -- Lecture #21

15

More Detailed Pipeline

- Examine flow through pipeline for `lw`

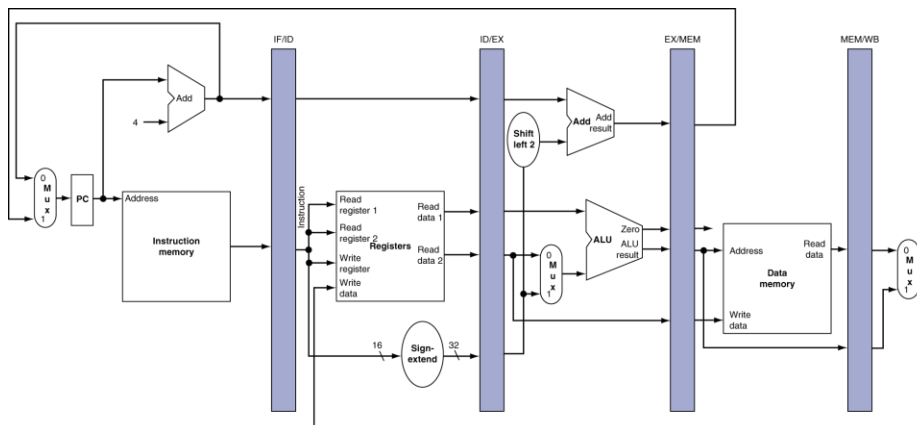


7/24/2012


Summer 2012 -- Lecture #21

17


Instruction Fetch (IF) for Load

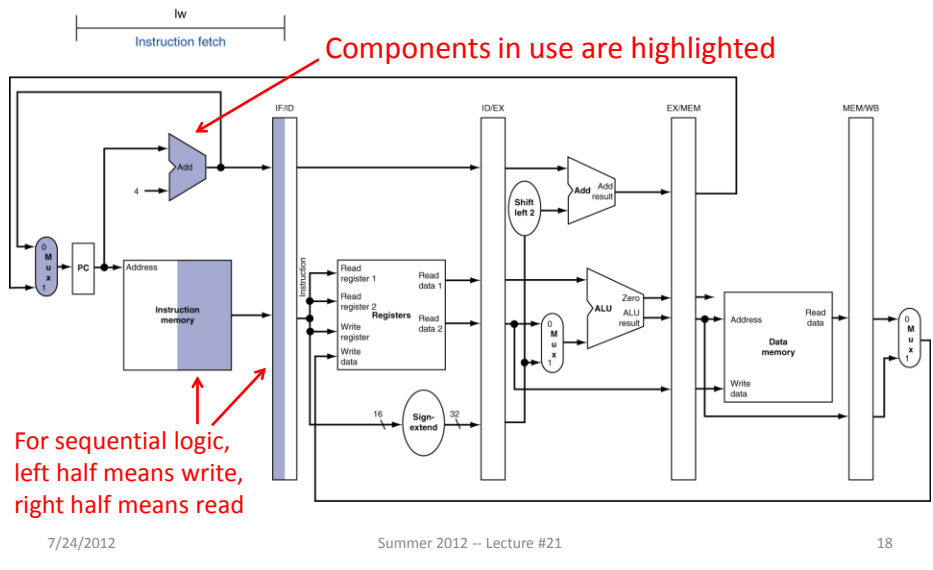


Instruction Decode (ID) for Load

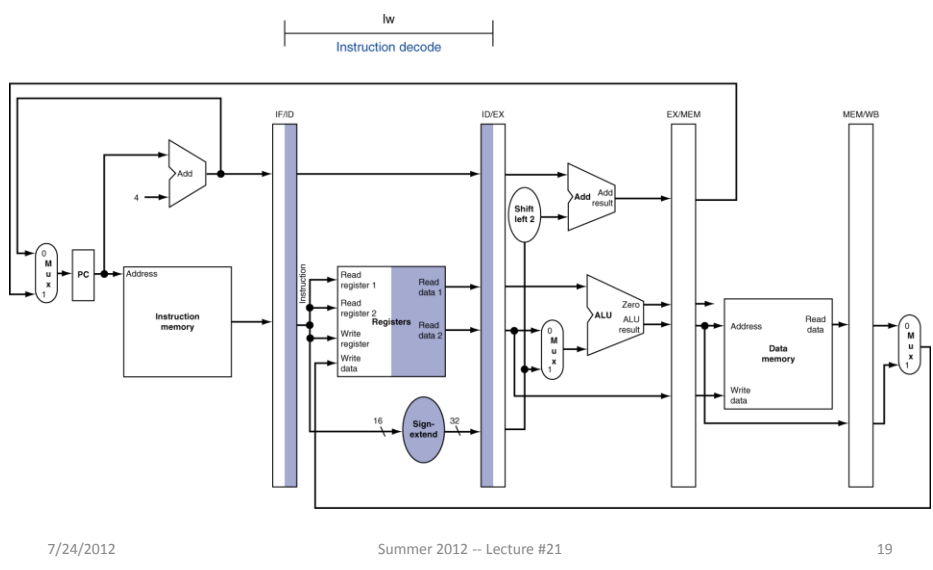

Execute (EX) for Load

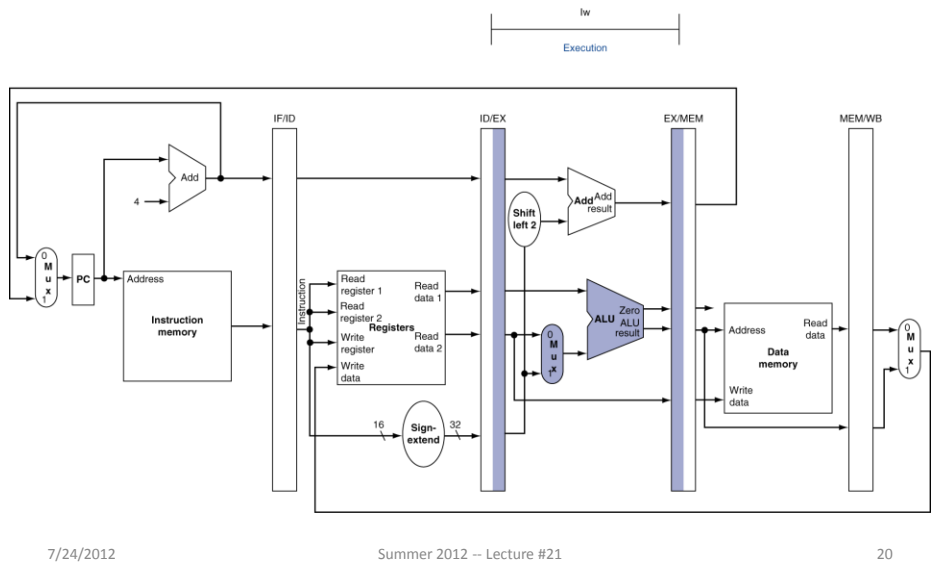


Memory (MEM) for Load

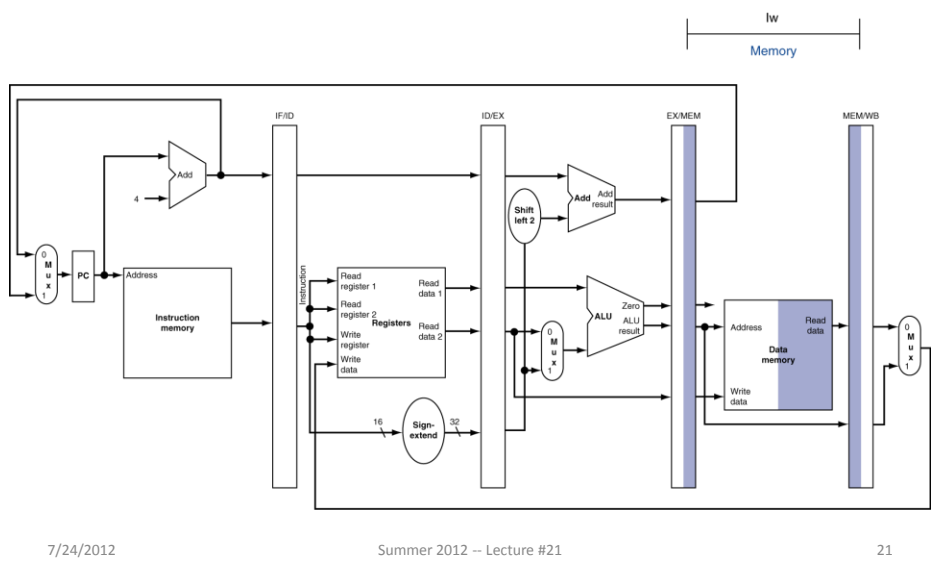


Write Back (WB) for Load

 There's something wrong here! (Can you spot it?)




Corrected Datapath

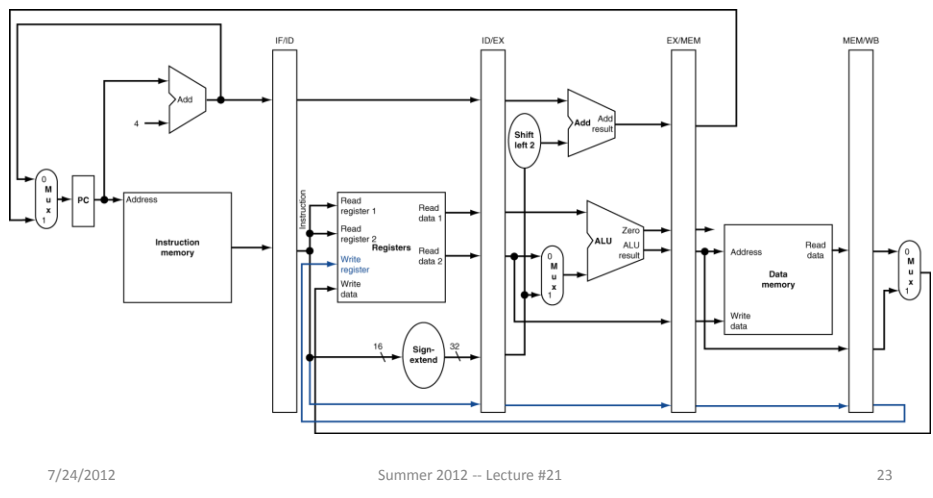- Now any instruction that writes to a register will work properly



Pipelined Execution Representation

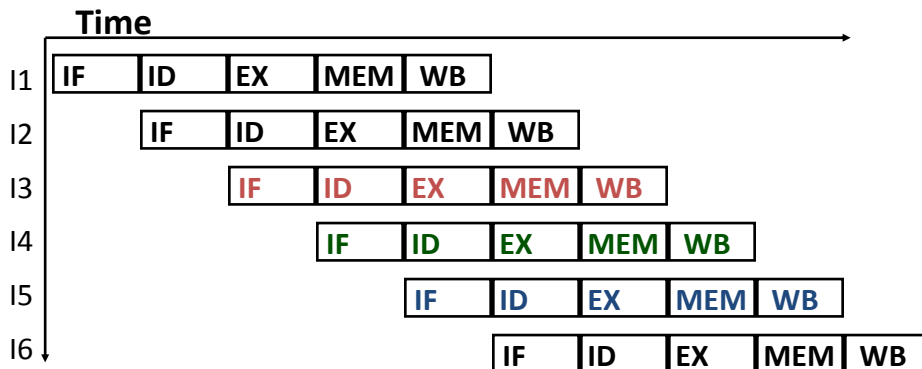

- Every instruction must take same number of steps, so some will idle
 - e.g. MEM stage for any arithmetic instruction

7/24/2012

Summer 2012 -- Lecture #21

24

时钟驱动的流水线时空图

- 本图用途：需精确分析指令/时间/流水线三者关系时
 - ◆ 行：某个时钟，指令流分别处于哪些阶段
 - ◆ 列：某个部件，在时间方向上的执行了哪些指令
- 注意区分流水阶段与流水线寄存器的关系
- 可以看出，在CLK5后，流水线全部充满
 - ◆ 所有部件都在执行指令
 - 只是不同的指令


				IF级	ID/RF级	EX级	MEM级	WB级	
相对PC的地址偏移	指令	CLK	PC	IM	IF/ID	ID/EX	EX/MEM	MEM/WB	RF
0	Instr 1	↑ 1	0→4	Instr 1	Instr 1				
4	Instr 2	↑ 2	4→8	Instr 2	Instr 2	Instr 1			
8	Instr 3	↑ 3	8→12	Instr 3	Instr 3	Instr 2	Instr 1		
12	Instr 4	↑ 4	12→16	Instr 4	Instr 4	Instr 3	Instr 2	Instr 1	
16	Instr 5	↑ 5	16→20	Instr 5	Instr 5	Instr 4	Instr 3	Instr 2	Instr 1
20	Instr 6	↑ 6	20→24	Instr 6	Instr 6	Instr 5	Instr 4	Instr 3	Instr 2

25




北京航空航天大学计算机学院
School of Computer Science and Engineering, Beihang University

Graphical Pipeline Diagrams

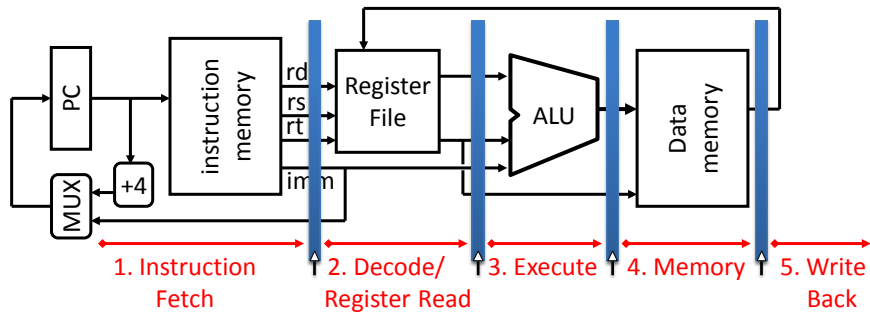

 - Use datapath figure below to represent pipeline:




7/24/2012

Summer 2012 -- Lecture #21

26

Graphical Pipeline Representation

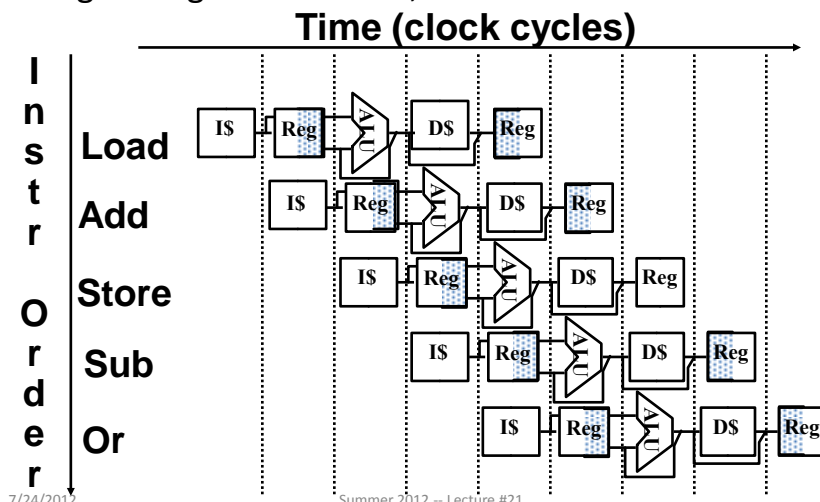- RegFile: right half is read, left half is write




7/24/2012

Summer 2012 -- Lecture #21

27


Instruction Level Parallelism (ILP)

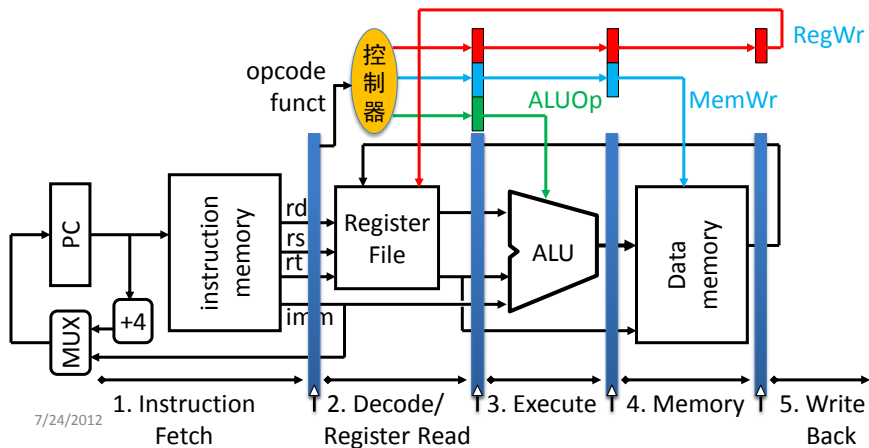- Pipelining allows us to execute parts of multiple instructions at the same time using the same hardware!
 - This is known as *instruction level parallelism*



Graphical Pipeline Representation

- RegFile: right half is read, left half is write

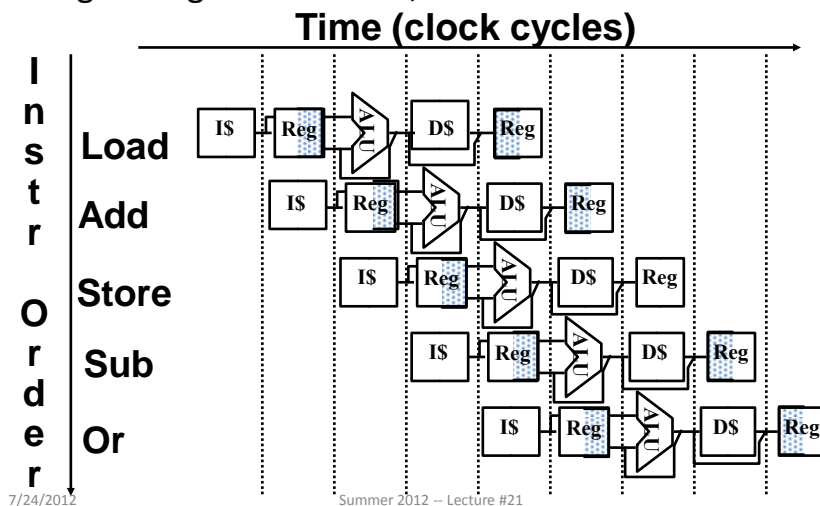

Summer 2012 -- Lecture #21

29

Pipeline Performance (1/2)

- Assume time for stages is
 - 100ps for register read or write
 - 200ps for other stages

Instr	Instr fetch	Register read	ALU op	Memory access	Register write	Total time
lw	200ps	100 ps	200ps	200ps	100 ps	800ps
sw	200ps	100 ps	200ps	200ps		700ps
R-format	200ps	100 ps	200ps		100 ps	600ps
beq	200ps	100 ps	200ps			500ps



- What is pipelined clock rate?
 - Compare pipelined datapath with single-cycle datapath

7/24/2012

Summer 2012 -- Lecture #21

30

Pipeline Performance (2/2)

 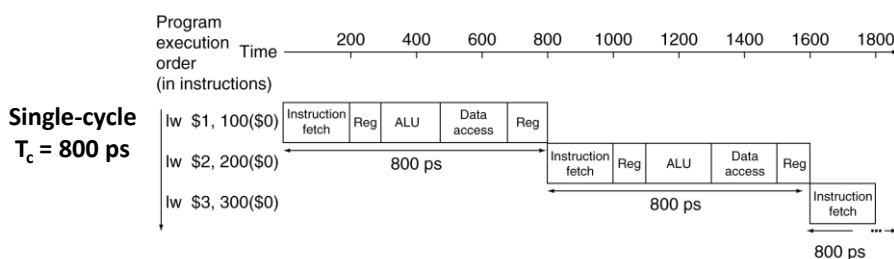

7/24/2012

Summer 2012 -- Lecture #21

31

Pipeline Speedup

- Use T_c (“time between completion of instructions”) to measure speedup
 - $T_{c, \text{pipelined}} \geq \frac{T_{c, \text{single-cycle}}}{\text{Number of stages}}$
 - Equality only achieved if stages are *balanced* (i.e. take the same amount of time)
- If not balanced, speedup is reduced
- Speedup due to increased throughput
 - Latency for each instruction does not decrease

7/24/2012

Summer 2012 -- Lecture #21

32

Pipelining and ISA Design

- MIPS Instruction Set designed for pipelining!
- All instructions are 32-bits
 - Easier to fetch and decode in one cycle
- Few and regular instruction formats, 2 source register fields always in same place
 - Can decode and read registers in one step
- Memory operands only in Loads and Stores
 - Can calculate address 3rd stage, access memory 4th stage
- Alignment of memory operands
 - Memory access takes only one cycle

7/24/2012


Summer 2012 -- Lecture #21

33



Question: Which of the following signals (buses or control signals) for MIPS-lite does NOT need to be passed into the EX pipeline stage?

- ☐ PC + 4
- ☐ MemWr
- ☐ RegWr
- ☐ imm16

 

34

第十六讲

Pipelining Hazards

A *hazard* is a situation that prevents starting the next instruction in the next clock cycle

1) *Structural hazard*

- A required resource is busy (e.g. needed in multiple stages)

2) *Data hazard*

- Data dependency between instructions
- Need to wait for previous instruction to complete its data read/write

3) *Control hazard*

- Flow of execution depends on previous instruction

7/25/2012

Summer 2012 -- Lecture #22

36

Agenda

- **Structural Hazards**
- Data Hazards
 - Forwarding
- Data Hazards (Continued)
 - Load Delay Slot
- Control Hazards
 - Branch and Jump Delay Slots
 - ~~Branch Prediction~~

7/25/2012

Summer 2012 -- Lecture #22

37

1. Structural Hazards


- Conflict for use of a resource
- MIPS pipeline with a single memory?
 - Load/Store requires memory access for data
 - Instruction fetch would have to *stall* for that cycle
 - Causes a pipeline “*bubble*”
- Hence, pipelined datapaths require separate instruction/data memories
 - Separate L1 I\$ and L1 D\$ take care of this

7/25/2012

Summer 2012 -- Lecture #22

38

Structural Hazard #1: Single Memory

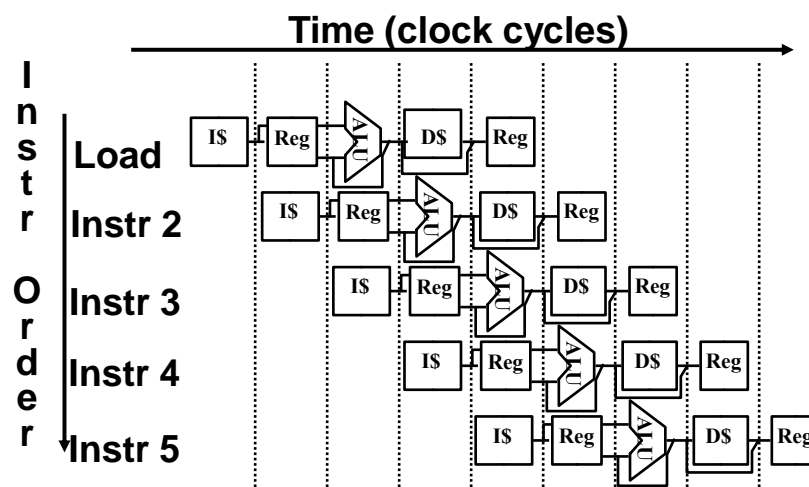


7/25/2012

Summer 2012 -- Lecture #22

39

Structural Hazard #2: Registers (1/2)

 

7/25/2012

Summer 2012 -- Lecture #22

40

Structural Hazard #2: Registers (2/2)

- Two different solutions have been used:
 - 1) Split RegFile access in two: Write during 1st half and Read during 2nd half of each clock cycle
 - Possible because RegFile access is *VERY* fast (takes less than half the time of ALU stage)
 - 2) Build RegFile with independent read and write ports
- **Conclusion:** Read and Write to registers during same clock cycle is okay

7/25/2012

Summer 2012 -- Lecture #22

41

Agenda


- Structural Hazards
- Data Hazards
 - Forwarding
- Data Hazards (Continued)
 - Load Delay Slot
- Control Hazards
 - Branch and Jump Delay Slots
 - Branch Prediction

7/25/2012

Summer 2012 -- Lecture #22


42

数据冒险

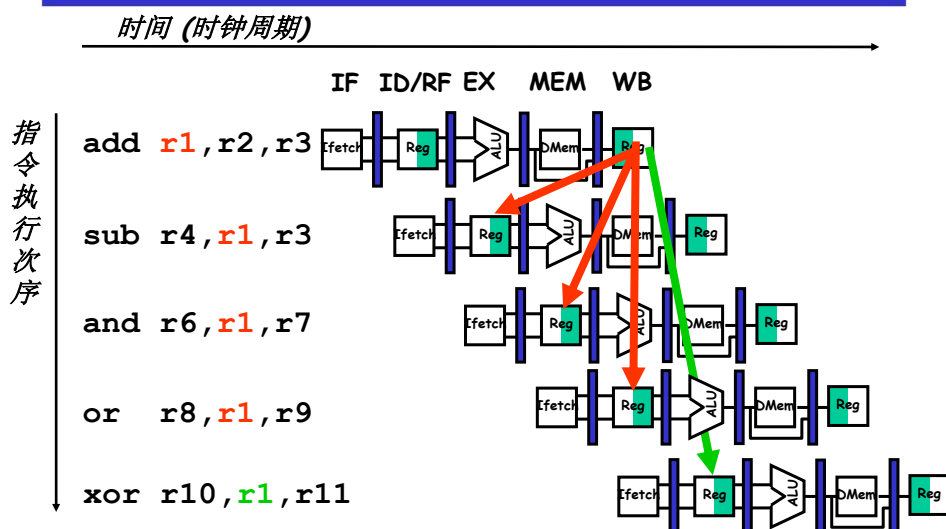


43

数据冒险解决策略—旁路

 


调整硬件结构支持旁路

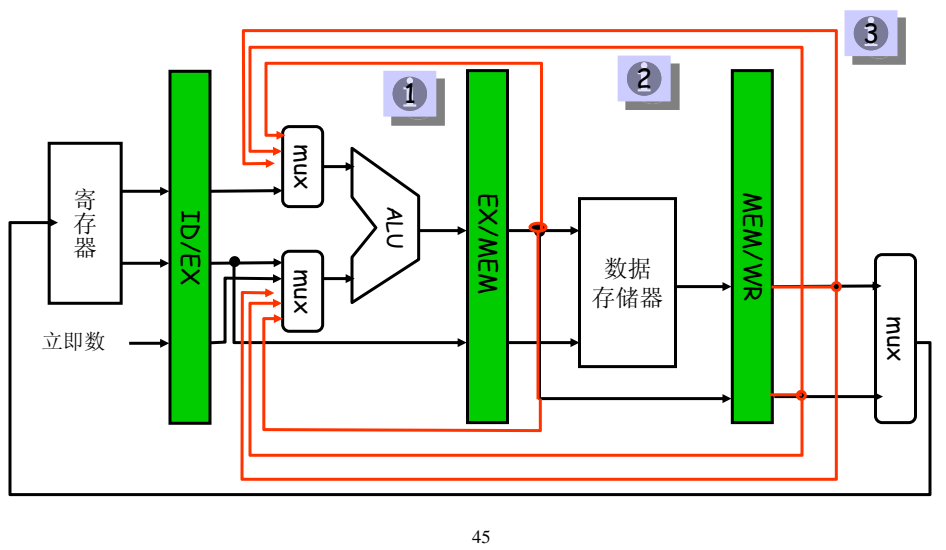

Datapath for Forwarding

- Handled by *forwarding unit*

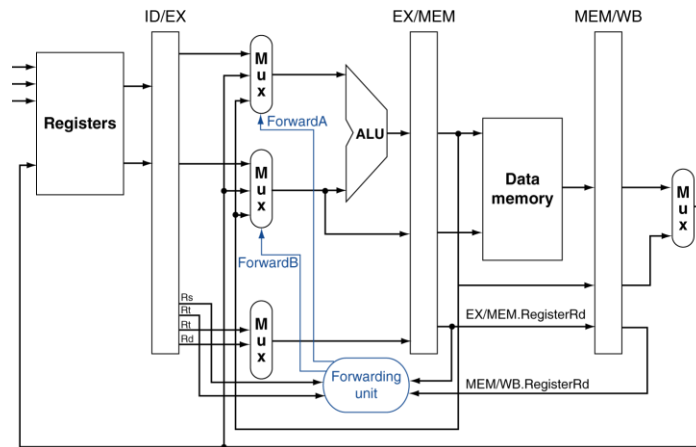

7/25/2012

Summer 2012 -- Lecture #22

46

Agenda

- Structural Hazards
- Data Hazards
 - Forwarding
- Data Hazards (Continued)**
 - Load Delay Slot**
- Control Hazards
 - Branch and Jump Delay Slots
 - Branch Prediction


7/25/2012

Summer 2012 -- Lecture #22

47

Data Hazard: Loads (1/4)

 - **Recall:** Dataflow backwards in time are hazards



- Can't solve all cases with forwarding
 - Must *stall* instruction dependent on load, then forward (more hardware)

7/25/2012


Summer 2012 -- Lecture #22

48

Data Hazard: Loads (2/4)

- *Hardware* stalls pipeline
 - Called “hardware interlock”

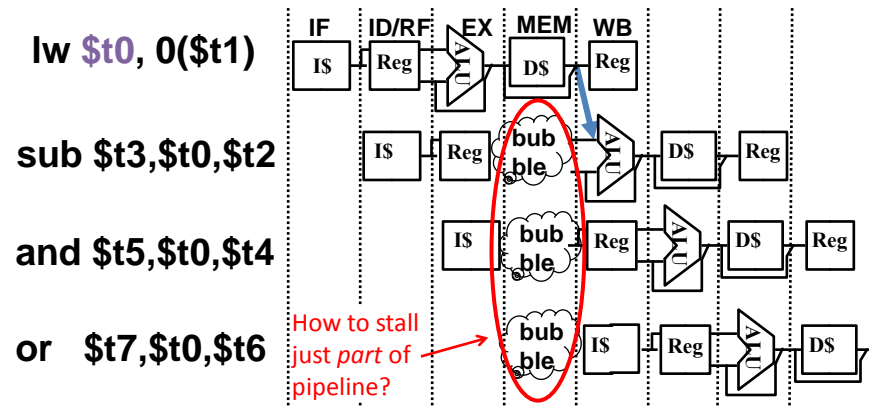Schematically, this is what we want, but in reality stalls done “horizontally”



7/25/2012

Summer 2012 -- Lecture #22

49

Data Hazard: Loads (3/4)

- Stall is equivalent to `nop`


`lw $t0, 0($t1)`

nop

`sub $t3,$t0,$t2`

`and $t5,$t0,$t4`

`or $t7,$t0,$t6`

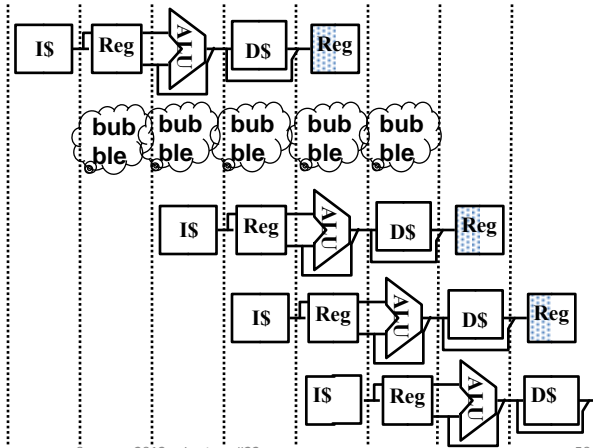

7/25/2012

Summer 2012 -- Lecture #22

50

load导致的数据冒险：Clk1上升沿后

指令流

- ◆ `lw` 进入流水线寄存器 IF/ID

- ◆ PC: 指向 `sub` 指令的地址

- $PC \leftarrow PC + 4$

- ◆ IM: 输出 `sub` 指令

后续不再分析PC和IM

		IF级			ID级	EX级	MEM级	WB级	
地址	指令	CLK	PC	IM	IF/ID	ID/EX	EX/MEM	MEM/WB	RF
0	lw \$t0, 0(\$t1)	↑ 1	0→4	lw→sub	lw				
4	sub \$t3, \$t0, \$t2								
8	and \$t5, \$t0, \$t4								
12	or \$t7, \$t0, \$t6								
16	add \$t1, \$t2, \$t3								

51



北京航空航天大学计算机学院
School of Computer Science and Engineering, Beihang University

load导致的数据冒险：Clk2上升沿后

指令流

- ◆ sub进入IF/ID寄存器；lw进入ID/EX寄存器

冲突分析：冲突出现

执行动作：设置控制信号，在clk3插入nop指令

- ◆ ①冻结IF/ID：sub继续被保存
- ◆ ②清除ID/EX：指令全为0，等价于插入NOP
- ◆ ③禁止PC：防止PC继续计数，PC应保持为PC+4

		IF级		ID级	EX级	MEM级	WB级		
地址	指令	CLK	PC	IM	IF/ID	ID/EX	EX/MEM	MEM/WB	RF
0	lw \$t0, 0(\$t1)	↑ 1	0→4	lw→sub	lw				
4	sub \$t3, \$t0, \$t2	↑ 2	4→8	sub→and	sub	lw			
8	and \$t5, \$t0, \$t4								
12	or \$t7, \$t0, \$t6								
16	add \$t1, \$t2, \$t3								

52



北京航空航天大学计算机学院
School of Computer Science and Engineering, Beihang University

load导致的数据冒险：Clk3上升沿后

指令流

- ◆ lw进入EX/MEM
- ◆ ID/EX向ALU提供数据

冲突分析：冲突解除

- ◆ 转发机制将在clk4时可以发挥作用

		IF级		ID级	EX级	MEM级	WB级		
地址	指令	CLK	PC	IM	IF/ID	ID/EX	EX/MEM	MEM/WB	RF
0	lw \$t0, 0(\$t1)	↑ 1	0→4	lw→sub	lw				
4	sub \$t3, \$t0, \$t2	↑ 2	4→8	sub→and	sub	lw			
8	and \$t5, \$t0, \$t4	↑ 3	8→8	and	sub	nop	lw		
12	or \$t7, \$t0, \$t6								
16	add \$t1, \$t2, \$t3								

53



北京航空航天大学计算机学院
School of Computer Science and Engineering, Beihang University

load导致的数据冒险：Clk4上升沿后

□ 指令流

- ◆ lw: 结果存入MEM/WB。
- ◆ sub: 进入ID/EX。故ALU的操作数可以从MEM/WB转发

□ 执行动作

- ◆ 控制MUX, 使得MEM/WB输入到ALU

		IF级		ID级	EX级	MEM级	WB级		
地址	指令	CLK	PC	IM	IF/ID	ID/EX	EX/MEM	MEM/WB	RF
0	lw \$t0, 0(\$t1)	↑ 1	0→4	lw→sub	lw				
4	sub \$t3, \$t0, \$t2	↑ 2	4→8	sub→and	sub	lw			
8	and \$t5, \$t0, \$t4	↑ 3	8→8	and	sub	nop	lw		
12	or \$t7, \$t0, \$t6	↑ 4	8→12	and→or	and	sub	nop	lw结果	
16	add \$t1, \$t2, \$t3								

54


 北京航空航天大学计算机学院
 School of Computer Science and Engineering, Beihang University

load导致的数据冒险：Clk5上升沿后

□ 指令流

- ◆ lw: 结果回写至RF
- ◆ sub: 结果保存在EX/MEM

		IF级		ID级	EX级	MEM级	WB级		
地址	指令	CLK	PC	IM	IF/ID	ID/EX	EX/MEM	MEM/WB	RF
0	lw \$t0, 0(\$t1)	↑ 1	0→4	lw→sub	lw				
4	sub \$t3, \$t0, \$t2	↑ 2	4→8	sub→and	sub	lw			
8	and \$t5, \$t0, \$t4	↑ 3	8→8	and	sub	nop	lw		
12	or \$t7, \$t0, \$t6	↑ 4	8→12	and→or	and	sub	nop	lw结果	
16	add \$t1, \$t2, \$t3	↑ 5	12→16	or→add	or	and	sub结果	nop	lw结果


55


 北京航空航天大学计算机学院
 School of Computer Science and Engineering, Beihang University

load导致的数据冒险

□ Q: 如果设置从DM到ALU输入的转发, 优劣如何?

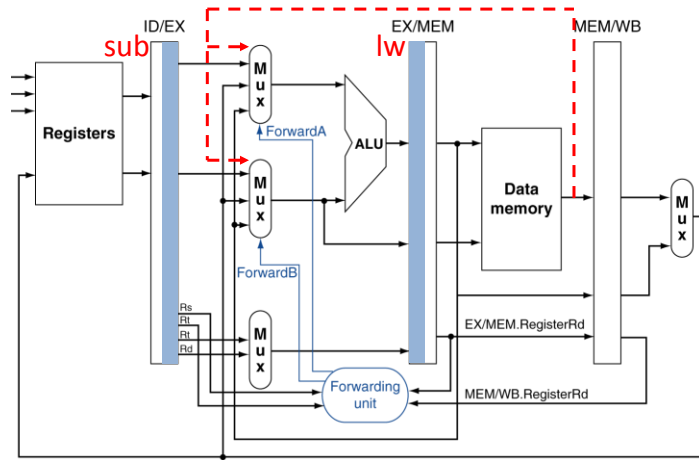- ◆ 设计初衷: 将DM读出数据提前1个clock转发至ALU, 从而消除lw指令导致的数据相关, 无需插入NOP



学计算机学院
Engineering, Beihang University


load导致的数据冒险

□ A: 这样做功能虽正确, 但是, CPU时钟频率大幅度降低

- ◆ 原设计: $f = 5\text{GHz}$
 - 各阶段最大延迟为200ps
- ◆ 新设计: $f = 2.5\text{GHz}$
 - EX阶段修改后 = ALU延迟 + DM延迟 = 400ps
 - EX阶段延迟成为最大延迟

警惕: 木桶原理!

流水线各阶段延迟不均衡, 将导致流水线性能严重下降

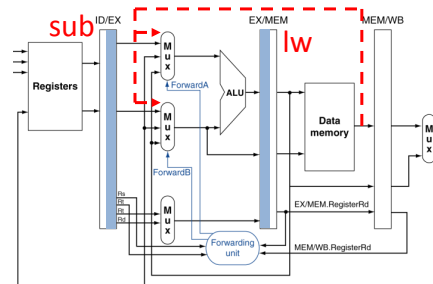

前面PPT的数据

Instr fetch	Register read	ALU op	Memory access	Register write
200ps	100 ps	200ps	200ps	100 ps



北京航空航天大学计算机学院
School of Computer Science and Engineering, Beihang University


如何插入NOP指令？

- 检测条件：IF/ID的前序是lw指令，并且lw的rt寄存器与IF/ID的rs或rt相同
- 执行动作：
 - ◆ ①冻结IF/ID：sub继续被保存
 - ◆ ②清除ID/EX：指令全为0，等价于插入NOP
 - ◆ ③禁止PC：防止PC继续计数，PC应保持为PC+4

地址 指令

```

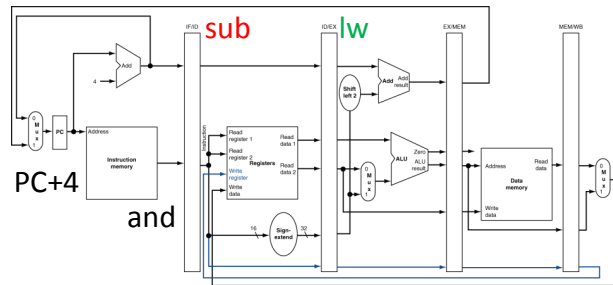0  lw  $t0, 0($t1)
4  sub  $t3, $t0, $t2
8  and  $t5, $t0, $t4
12 or  $t7, $t0, $t6
16 add  $t1, $t2, $t3
  
```



58

北京航空航天大学计算机学院
School of Computer Science and Engineering, Beihang University


如何插入NOP指令？

Cycle N


地址 指令

```

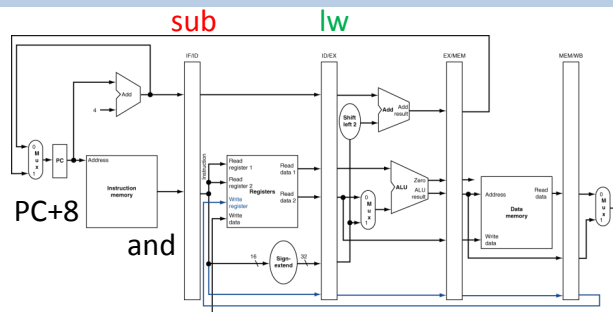0  lw  $t0, 0($t1)
4  sub  $t3, $t0, $t2
8  and  $t5, $t0, $t4
12 or  $t7, $t0, $t6
16 add  $t1, $t2, $t3
  
```



Cycle N+1

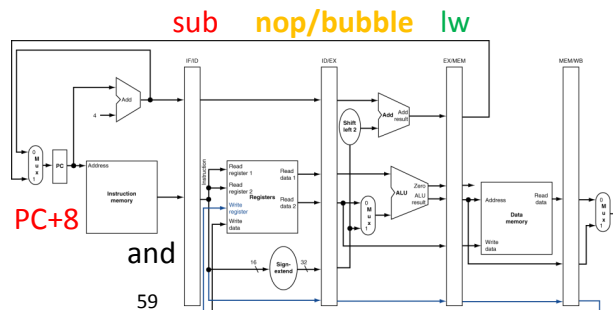


59

如何插入NOP指令？

- 执行动作：
 - ◆ ①冻结IF/ID: sub继续被保存
 - ◆ ②清除ID/EX: 指令全为0, 等价于插入NOP
 - ◆ ③禁止PC: 防止PC继续计数, PC应保持为PC+4
- 数据通路: 将IF/ID修改为使能型寄存器
- 控制系统: 增加IF/ID.en控制信号
 - ◆ 当IF/ID.en为0时, IF/ID在下个clock上升沿到来时保持不变


使能型
寄存器

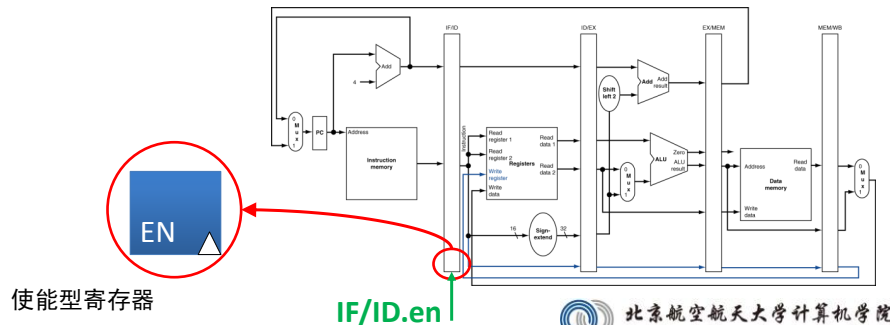

如何插入NOP指令？

- 执行动作：
 - ◆ ①冻结IF/ID: sub继续被保存
 - ◆ ②清除ID/EX: 指令全为0, 等价于插入NOP
 - ◆ ③禁止PC: 防止PC继续计数, PC应保持为PC+4
- 数据通路: 将ID/EX修改为复位型寄存器
- 控制系统: 增加ID/EX.clr控制信号
 - ◆ 当ID/EX.clr为0时, ID/EX在下个clock上升沿到来时被清除为0

复位型
寄存器

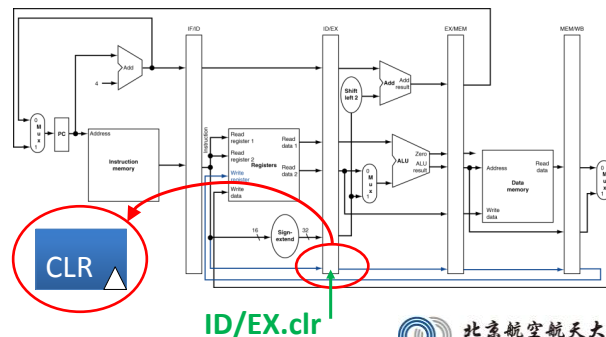

如何插入NOP指令？



■ 执行动作：


- ◆ ①冻结IF/ID：sub继续被保存
- ◆ ②清除ID/EX：指令全为0，等价于插入NOP
- ◆ ③禁止PC：防止PC继续计数，PC应保持为PC+4

使能型寄存器

■ 数据通路：将PC修改为使能型寄存器

■ 控制系统：增加PC.en控制信号

- ◆ 当PC.en为0时，PC在下一个clock上升沿到来时保持不变

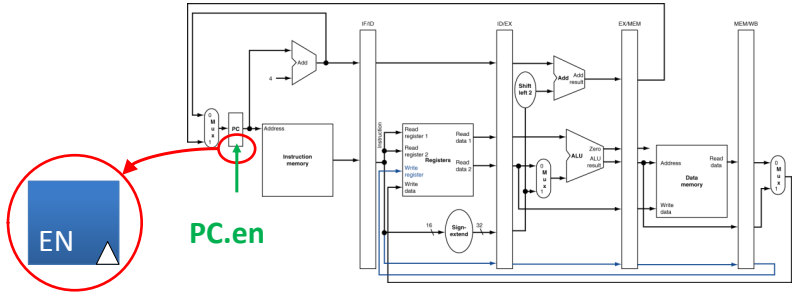

62

如何插入NOP指令？

■ lw冒险处理示例伪代码

■ 注意：时序关系

- ◆ 各信号在clk2上升沿后有效
- ◆ NOP是在clk3上升沿后发生，即寄存器值在clk3上升沿到来时发生变化(或保持不变)

```
if (ID/EX.MemRead) &
  ((ID/EX.rt == IF/ID.rs) |
   (ID/EX.rt == IF/ID.rt))
  IF/ID.en ← 禁止
  ID/EX.clr ← 清除
  PC.en ← 禁止
```

				IF级	ID级	EX级	MEM级	WB级	
地址	指令	CLK	PC	IM	IF/ID	ID/EX	EX/MEM	MEM/WB	RF
0	lw \$t0, 0(\$t1)	↑ 1	0→4	lw→sub	lw				
4	sub \$t3, \$t0, \$t2	↑ 2	4→8	sub→and	sub	lw			
8	and \$t5, \$t0, \$t4	↑ 3	8→8	and	sub	nop	lw		
12	or \$t7, \$t0, \$t6								
16	add \$t1, \$t2, \$t3								

如果没有转发电路呢？

- 由于有转发电路，因此lw指令只插入1个NOP指令
- Q: 如果没有转发，需要怎么处理呢？
- A: EX/MEM, MEM/WB也均需要做冲突分析及NOP处理
 - ◆ EX/MEM, MEM/WB也需修改，并增加相应控制信号


				IF级	ID级	EX级	MEM级	WB级	
地址	指令	CLK	PC	IM	IF/ID	ID/EX	EX/MEM	MEM/WB	RF
0	lw \$t0, 0(\$t1)	↑ 1	0→4	lw→sub	lw				
4	sub \$t3, \$t0, \$t2	↑ 2	4→8	sub→and	sub	lw			
8	and \$t5, \$t0, \$t4	↑ 3	8	and	sub	nop	lw		
12	or \$t7, \$t0, \$t6	↑ 4	8	and	sub	nop	nop	lw结果	
16	add \$t1, \$t2, \$t3	↑ 5	8	and	sub	nop	nop	nop	lw结果
		↑ 6	8→12	and→or	and	sub	nop	nop	nop

Data Hazard: Loads (4/4)

- Slot after a load is called a *load delay slot*
 - If that instruction uses the result of the load, then the hardware interlock will stall it for one cycle
 - Letting the hardware stall the instruction in the delay slot is equivalent to putting a `nop` in the slot (except the latter uses more code space)
- **Idea:** Let the compiler put an unrelated instruction in that slot → no stall!

Code Scheduling to Avoid Stalls

 - Reorder code to avoid use of load result in the next instruction!
- MIPS code for $A=B+E$; $C=B+F$;



7/25/2012

Summer 2012 -- Lecture #22

66

Agenda

- Structural Hazards
- Data Hazards
 - Forwarding
- Data Hazards (Continued)
 - Load Delay Slot
- Control Hazards
 - Branch and Jump Delay Slots
 - Branch Prediction

7/25/2012

Summer 2012 -- Lecture #22

67

3. Control Hazards

- Branch (beq, bne) determines flow of control
 - Fetching next instruction depends on branch outcome
 - Pipeline can't always fetch correct instruction
 - Still working on ID stage of branch
- **Simple Solution:** Stall on *every* branch until we have the new PC value
 - How long must we stall?

7/25/2012

Summer 2012 -- Lecture #22


68

B指令冒险造成的停顿代价

地址	指令								
		CLK	PC	IF级	ID级	EX级	MEM级	WB级	RF
0	beq \$1, \$3, 24	1	0→4	beq→and	beq				
4	and \$12, \$2, \$5	2	4	and	nop	beq			
8	or \$13, \$6, \$2	3	4	and	nop	nop	beq结果		
12	add \$14, \$2, \$2	4	4→28	and→lw	nop	nop	nop		
		5	28→32	lw→XX	lw	nop	nop	nop	nop
28	lw \$4, 50(\$7)								

□ 如不对B指令做任何处理，则必须插入3个NOP

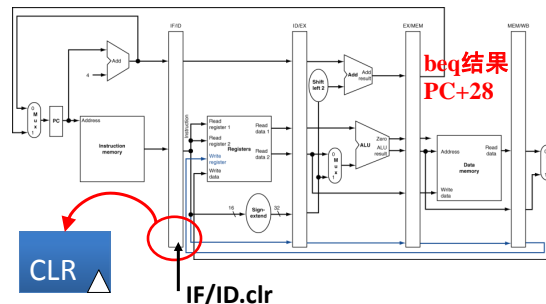- b指令结果及新PC值保存在EX/MEM，因此PC在clk4才能加载正确值
- IF/ID在clk5才能存入转移后指令(即lw指令)



69




北京航空航天大学计算机学院
School of Computer Science and Engineering, Beihang University

方案1：假定分支不发生


- 即使在ID级发现是B指令也不停顿
- 根据B指令结果，决定是否清除3条后继指令
 - 使得and/or/add不能前进

PC相对偏移	指令
0	beq \$1, \$3, 24
4	and \$12, \$2, \$5
8	or \$13, \$6, \$2
12	add \$14, \$2, \$2
28	lw \$4, 50(\$7)

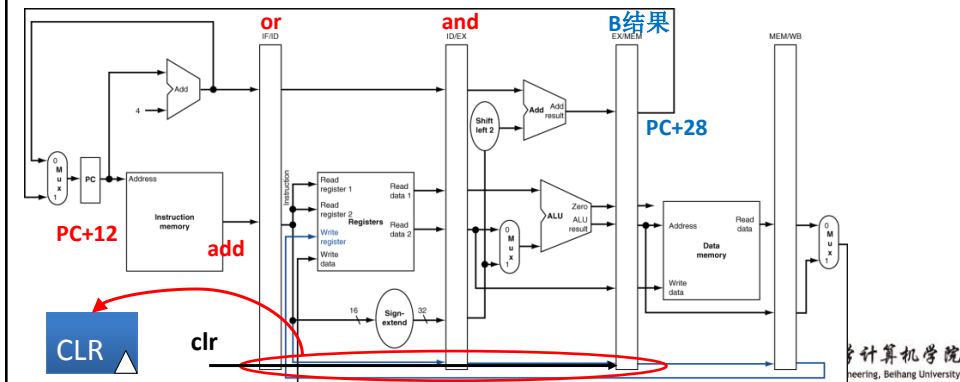

方案2：缩短分支延迟

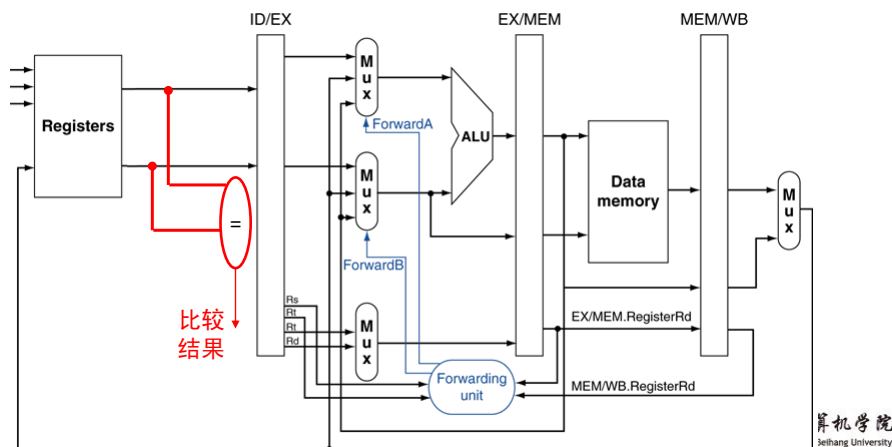- 在ID阶段放置比较器，尽快得到B指令结果
 - B指令结果可以提前2个clock得到
 - B指令后继可能被废弃的指令减少为1条
 - 当需要转移时，清除IF/ID即可



方案2：缩短分支延迟


- 比较器前置后，会产生数据相关
 - ◆ B指令可能依赖于前条指令的结果

Q: 如果依赖MEM/WB的结果，是否需要设置转发？

提示：MEM/WB已经有回写通道了，但RF设计满足吗？

- 依赖计算1：从ALU转发数据

- 依赖计算2：只能暂停

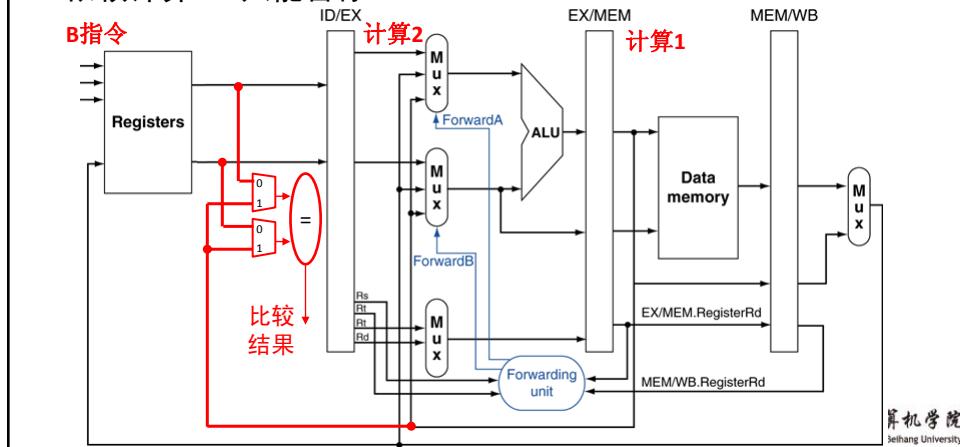

3. Control Hazard: Branching

- **Option #3: Branch delay slot**
 - Whether or not we take the branch, *always* execute the instruction immediately following the branch
 - Worst-Case: Put a `nop` in the branch-delay slot
 - Better Case: Move an instruction from before the branch into the branch-delay slot
 - Must not affect the logic of program

3. Control Hazard: Branching

- MIPS uses this *delayed branch* concept
 - Re-ordering instructions is a common way to speed up programs
 - Compiler finds an instruction to put in the branch delay slot
- Jumps also have a delay slot
 - Why is one needed?

7/25/2012

Summer 2012 -- Lecture #22

74

Delayed Branch Example

Nondelayed Branch

```

or   $8, $9, $10
add  $1, $2, $3
sub  $4, $5, $6
beq  $1, $4, Exit
xor  $10, $1, $11

```

Exit:

7/25/2012

Delayed Branch

```

add  $1, $2, $3
sub  $4, $5, $6
beq  $1, $4, Exit
or   $8, $9, $10
xor  $10, $1, $11

```

Exit:

Why not any of the
other instructions?

Summer 2012 -- Lecture #22

75

Delayed Jump in MIPS

- MIPS Green Sheet for `jal`:
 $R[31] = PC + 8$; $PC = \text{JumpAddr}$
 - $PC+8$ because of *jump delay slot*!
 - Instruction at $PC+4$ always gets executed before `jal` jumps to label, so return to $PC+8$

7/25/2012

Summer 2012 -- Lecture #22

76

Question: For each code sequences below, choose one of the statements below:



1:

```
lw $t0, 0($t0)
add $t1, $t0, $t0
```

2:

```
add $t1, $t0, $t0
addi $t2, $t0, 5
addi $t4, $t1, 5
```


3:

```
addi $t1, $t0, 1
addi $t2, $t0, 2
addi $t3, $t0, 2
addi $t3, $t0, 4
addi $t5, $t1, 5
```

- ☐ No stalls as is
- ☐ No stalls with forwarding
- ☐ Must stall

77

Code Sequence 1

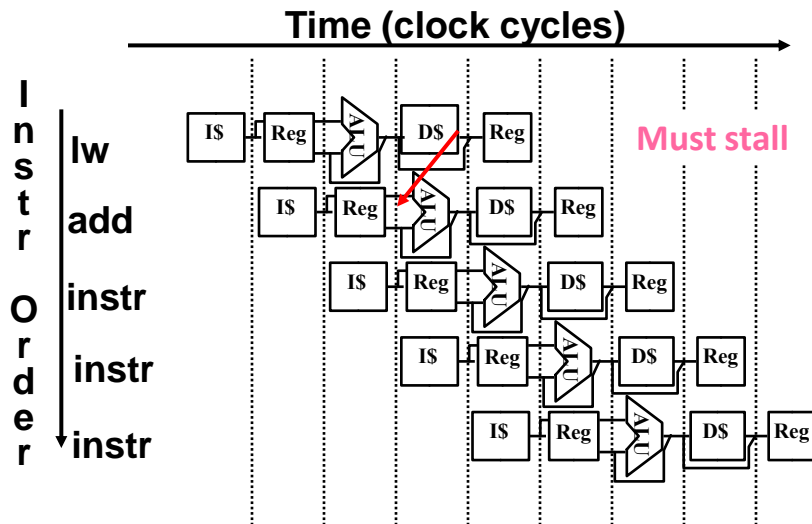


7/25/2012

Summer 2012 -- Lecture #22

78

Code Sequence 2

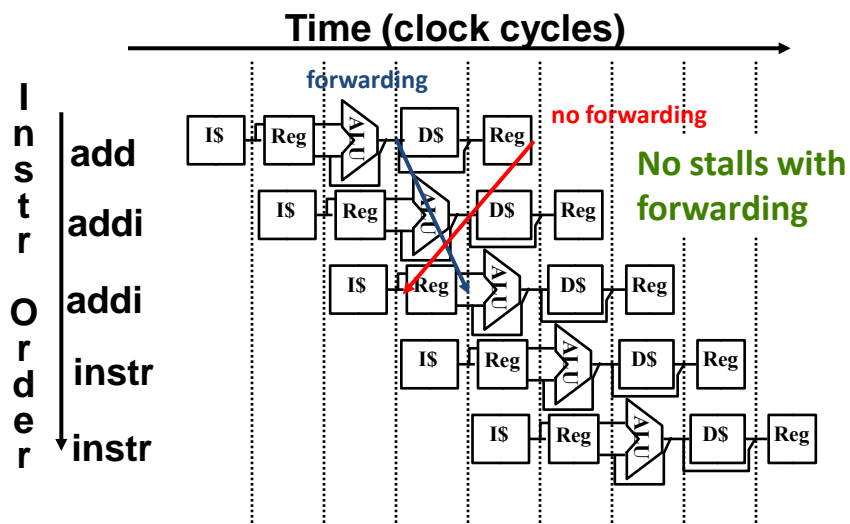


7/25/2012

Summer 2012 -- Lecture #22

79

Code Sequence 3

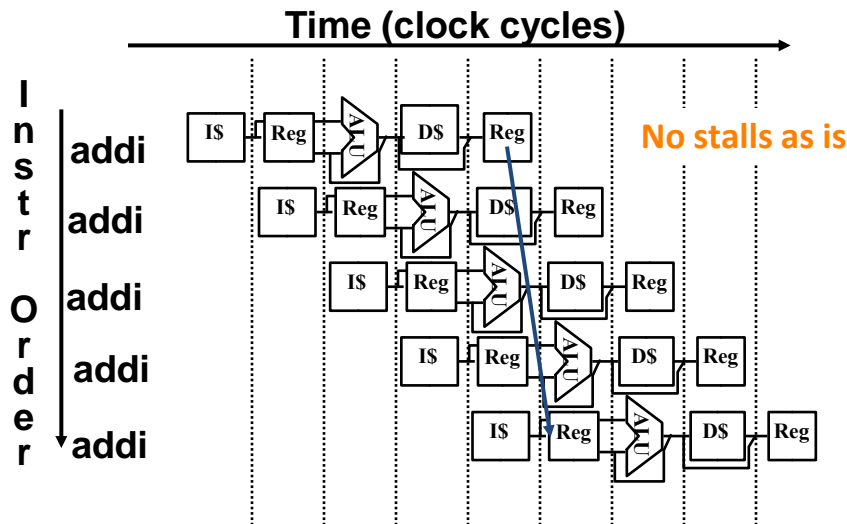

7/25/2012

Summer 2012 -- Lecture #22

80

Summary

- Hazards reduce effectiveness of pipelining
 - Cause stalls/bubbles
- Structural Hazards
 - Conflict in use of datapath component
- Data Hazards
 - Need to wait for result of a previous instruction
- Control Hazards
 - Address of next instruction uncertain/unknown
 - Branch and jump delay slots

7/25/2012

Summer 2012 -- Lecture #22

81